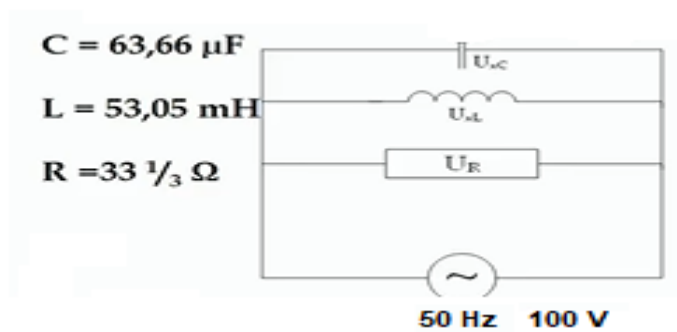



LCR -parallel



$$X_C = 1 / 2\pi f C = 1 / 2 \times 3.14 \times 50 \times 63.66 \times 10^{-6} = 50 \text{ Ohm}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 53.05 \times 10^{-3} = 16.66 \text{ Ohm}$$


$$R = 33.5 \text{ Ohm}$$

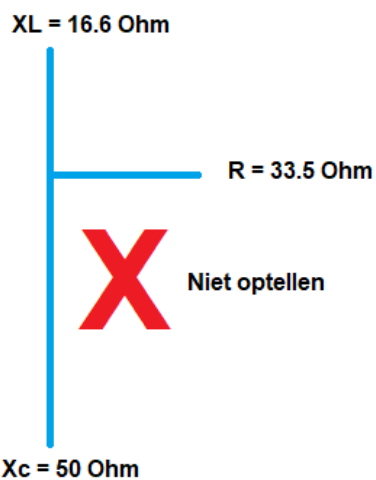

$$I_r = U / R = 100 / 33.5 = 3 \text{ A}$$

$$I_L = U / X_L = 100 / 16.6 = 6 \text{ A}$$
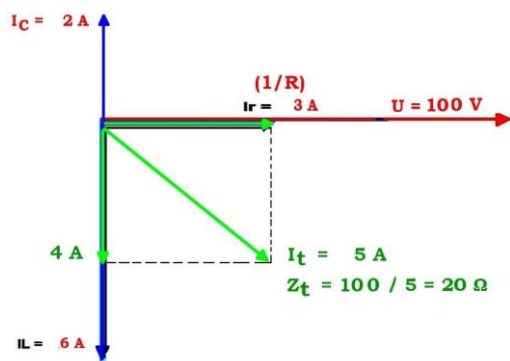
$$I_C = U / X_C = 100 / 50 = 2 \text{ A}$$



Vectordiagram by PA9JOO/P

$$I_t = \sqrt{I_r^2 + (I_L - I_C)^2} =$$

$$I_t = \sqrt{4^2 + 3^2} =$$

$$I_t = 5 \text{ A}$$

$$Z = U / I_t$$

$$Z = 100 / 5 = 20 \text{ Ohm}$$